

Using the **AD7150** Capacitance-to-Digital Converter for Proximity Sensing Applications

CIRCUIT FUNCTION AND BENEFITS

The circuit described in this document provides the basis for developing a proximity sensing application using the **AD7150** capacitance-to-digital converter (CDC).

The **AD7150** CDC measures the capacitance between two electrodes and compares the measurement result with a threshold value, which can either be fixed or dynamically adjusted by the on-chip, adaptive threshold algorithm engine.

If the input capacitance is altered, for example, by the presence of a hand, an output flag is set to indicate that a threshold has been exceeded, indicating proximity.

This on-chip, adaptive threshold algorithm engine also enables the **AD7150** to adapt to slow changes in the sensing capacitance, which can be caused by environmental changes, such as humidity or temperature, without losing the capability of proximity sensing.

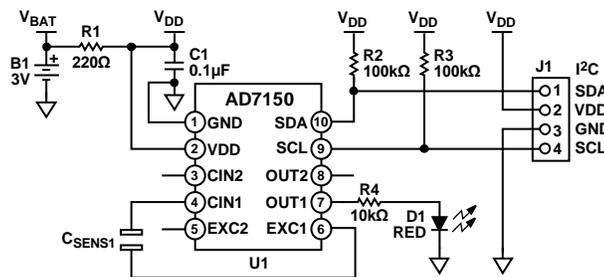


Figure 1. **AD7150** as a Proximity Detector in Standalone Operation

TABLE OF CONTENTS

Circuit Function and Benefits.....	1	Common Variations.....	3
Revision History	2	References.....	5
Circuit Description.....	3		

REVISION HISTORY

11/2017—Rev. 0 to Rev. A

Document Title Changed from CN0095 to AN-1528..... Universal Change to Figure 1	1
Changes to Circuit Description Section and Common Variations Section	3
Added Figure 4 and Figure 5; Renumbered Sequentially	4
Changes to Figure 3, Table 1, and Table 2	4
Changes to References Section	6

7/2009—Revision 0: Initial Version

CIRCUIT DESCRIPTION

A proximity sensing application using the [AD7150](#) in standalone operation requires very few peripheral components, as shown in Figure 1. The circuit requires a supply voltage (Battery B1), some filtering of the supply voltage (R1, C1), and weak pull-up resistors (R2 and R3) on the I²C-compatible input/output pins. The red LED (D1) provides a visual indicator that the [AD7150](#) has detected the proximity, for example, of a hand. The circuit requires a capacitive sensing element (C_{SENS1}), which can consist of two tracks on an FR4 printed circuit board (PCB), as shown in Figure 2.

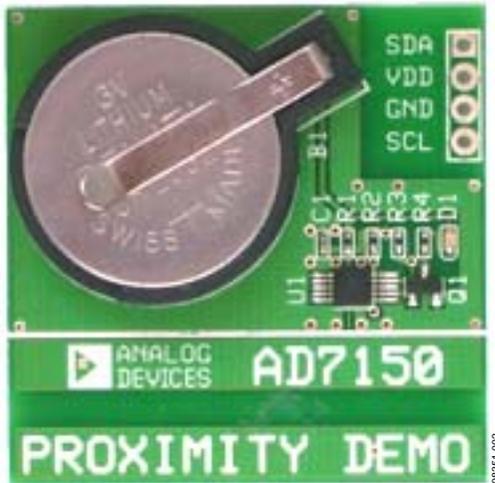


Figure 2. [AD7150](#) Proximity Detector Demonstration Board

COMMON VARIATIONS

Variations in the [AD7150](#) proximity circuit depend on the environment and the targeted application. For example, automotive applications must withstand a high level of electromagnetic current (EMC) noise and transient pulses at the system level; therefore, this type of application requires a suitable design for harsh electrical and physical environments.

The unique design of the [AD7150](#) for measuring floating capacitive sensors allows the user to place a filter structure in the capacitive front end. The filter structure (R1 to R6, C1 to C6), as shown in Figure 3, filters noise that is coupled into the electrodes of the sensor. The optional network consisting of R7, R8, C7, and C8 prevents noise from the external I²C-compatible interface from coupling back into the circuit.

Substantial EMC testing has been performed on the [AD7150](#). The results of the [AD7150](#) EMC performance can be found in the [AN-1011 Application Note, EMC Protection of the AD7150](#).

The excitation voltages (EXC1 and EXC2), which drive the capacitive sensors, are generated by circuits within the [AD7150](#). The VDD pin powers these circuits. A noisy supply voltage can result in unwanted noise signals on the capacitive input. The voltage supply circuit shown in Figure 3 uses the [ADP1720](#) low dropout (LDO) regulator, used in 3.3 V mode, to filter battery noise and suppress transient pulses in automotive applications.

If the outputs of the [AD7150](#) are not connected directly to a microcontroller, they can require conditioning to translate the voltage level and/or signal polarity. Typical conditioning circuits for the OUT1 and OUT2 pins are shown in Figure 3. The double diffused metal-oxide semiconductor (DMOS) field effect transistors (FETs), Q1 and Q2, act as open drain output drivers, and the 27 V varistors (V1 and V2) protect the circuitry from large external transients.

When connected to a microcontroller, some of the [AD7150](#) registers used by the on-chip adaptive threshold algorithm engine can be programmed to settings other than the power-up default settings. This programming is done via the I²C-compatible interface and enables the [AD7150](#) to be used for different applications with different requirements. See the [AD7150](#) data sheet for more details.

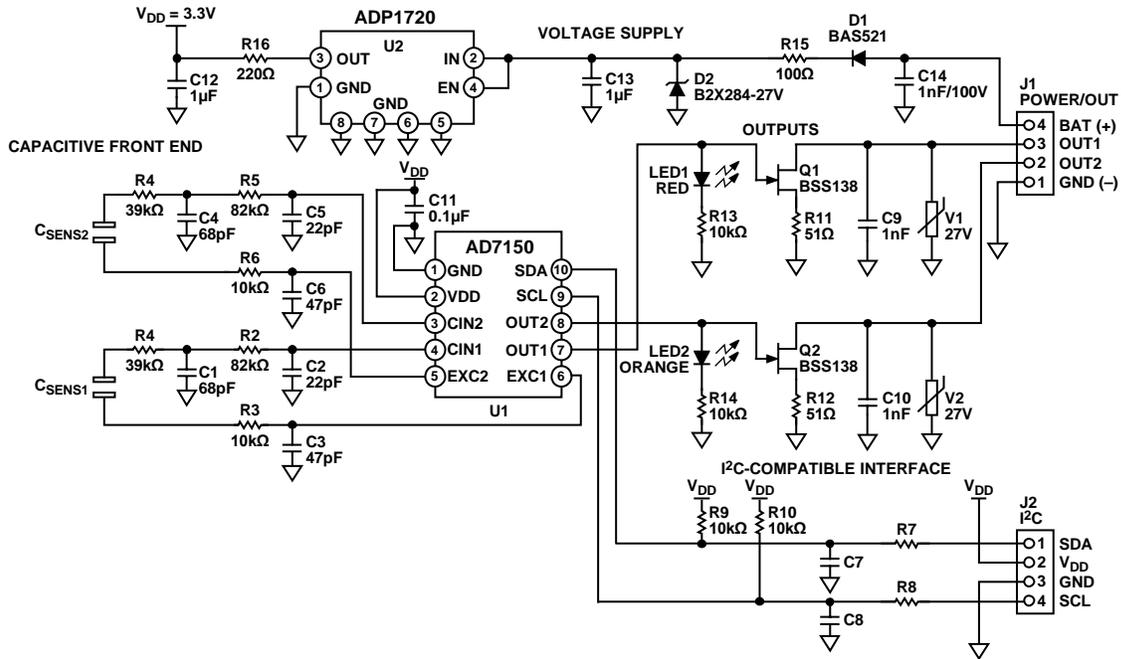


Figure 3. AD7150 in an Automotive Door Handle Application in Standalone Operation

Table 1 and Table 2 show a typical proximity performance of the door handle demonstration with different sensitivity and capacitive input range settings.

Table 1. Typical Proximity Performance of Sensor 1 on the Door Handle Demonstration Board (see Figure 4)

Capacitive Range (pF)	Threshold Sensitivity Setting	Maximum Proximity Detection (mm)
0.5	4	38
	8	31
	12	27
	16	24
2.0	4	25
	8	17
	12	12
	16	10

Table 2. Typical Proximity Performance of Sensor 2 on the Door Handle Demonstration Board (see Figure 5)

Capacitive Range (pF)	Threshold Sensitivity Setting	Maximum Proximity Detection (mm)
0.5	4	70
	8	58
	12	50
	16	45
2.0	4	45
	8	35
	12	28
	16	24

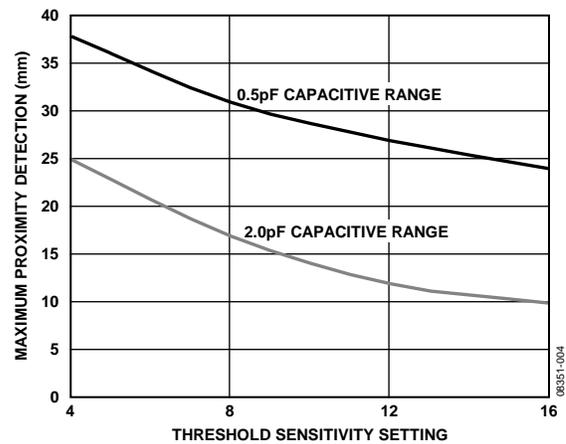


Figure 4. Typical Proximity Performance, Sensor 1

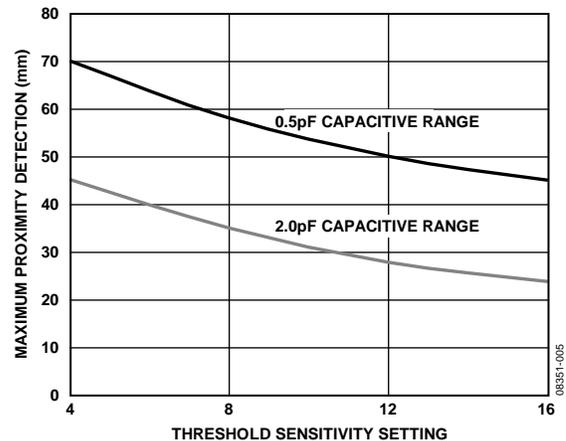


Figure 5. Typical Proximity Performance, Sensor 2

The unique design of the [AD7150](#) for measuring floating capacitive sensors makes the [AD7150](#) tolerant of parasitic capacitances to ground. This tolerance allows the use of ground planes to either shield the capacitive front-end signals from other analog or digital signals on the board, or to shield the signals from each other. Figure 6 shows the [AD7150](#) door handle demonstration board where Sensor 2 on the door handle demonstration board has a ground plane on the entire top layer to prevent proximity detection when a person leans against the door handle of a car. The sensor electrodes are placed on the bottom layer in the same way as shown for Sensor 1 (see Figure 6). Therefore, Sensor 2 only detects proximity when a hand reaches behind the door handle.

REFERENCES

- [AN-856 Application Note, AD7142 Applications Using Sensor Buttons](#), Analog Devices, Inc.
- [AN-925 Application Note, Sensors for the AD7147 and AD7148 CapTouch Controllers](#), Analog Devices.
- [AN-1011 Application Note, EMC Protection of the AD7150](#), Analog Devices.
- [MT-022 Tutorial, ADC Architectures III: Sigma-Delta ADC Basics](#), Analog Devices.
- [MT-023 Tutorial, ADC Architectures IV: Sigma-Delta ADC Advanced Concepts and Applications](#), Analog Devices.
- [MT-031 Tutorial, Grounding Data Converters and Solving the Mystery of AGND and DGND](#), Analog Devices.
- [MT-101 Tutorial, Decoupling Techniques](#), Analog Devices.



Figure 6. [AD7150](#) Door Handle Demonstration Board

I²C refers to a communications protocol originally developed by Philips Semiconductors (now NXP Semiconductors).